

Certificate


Certified that this is the bonafide work of ASMITA MANGIPUDI
(Student's Name)
of Class XII of SRI CHAITANYA SCHOOL
(Class/Section) (School's Name)


He/She has performed these experiments during the academic year 2023 - 2024

Number of practicals certified 8 out of 8
in PHYSICS.
(Subject's Name)

Candidate's Registration No. : 18615950

Batch No. : 1

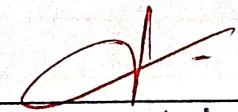
Teacher's Signature
Sri Chaitanya Techno School
90/10, 90/11, 93/2A3, 93/2A4
Beside Shannika Restaurant, CRR St, Aces Road
Marathahalli-2, Bengaluru - 560 037
Phone No: 9811012
School Code: 45546

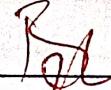
Examiner's Signature

Index

Name : ASMITA MANGIPUDI Class 12 Year 2024


Expt. No.	Date	Title of the Experiments	Page No.	Date of Submission	Remarks
1.	7.9.23	Resistivity of given wires by using ohm's law	02.	DA 18.8.23	
2.	21.9.23	Resistivity of a given wire by using meter bridge.	05	DA 18.8.23	
3.	5.10.23	Laws of combination of resistance in series by using meter bridge.	08	DA 18.8.23	
4.	15.10.23	Figure of merit of galvanometer by half deflection method.	11	DA 18.8.23	
5.	8.11.23	Refractive index of glass using travelling microscope.	14	DA 18.8.23	
6.	22.11.23	Refractive index of water by using convex lens.	14	DA 18.8.23	
7.	9.11.23	Angle of minimum deviation for a given prism.	20	DA 18.8.23	
8.	15.12.23	P-N Junction diode.	23	DA 18.8.23	

Index

Name : Class Year

<i>Expt. No.</i>	<i>Date</i>	<i>Title of the Experiments</i>	<i>Page No.</i>	<i>Date of Submission</i>	<i>Remarks</i>
0.1	8.10.23	ACTIVITY - 1 <i>Activity to find out which plant grows best in which soil</i>	10	10.10.23	80-01
0.2	12.10.23	ACTIVITY - 2 <i>Activity to find out which plant grows best in which soil</i>	10	12.10.23	80-01
0.3	19.10.23	ACTIVITY - 3 <i>Activity to find out which plant grows best in which soil</i>	10	19.10.23	80-01
0.4	2.11.23	ACTIVITY - 4 <i>Activity to find out which plant grows best in which soil</i>	10	2.11.23	80-01
0.5	19.11.23	ACTIVITY - 5 <i>Activity to find out which plant grows best in which soil</i>	10	19.11.23	80-01
0.6	26.11.23	ACTIVITY - 6 <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		III. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		IV. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		V. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		VI. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		VII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		VIII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		IX. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		X. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XI. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XIII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XIV. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XV. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XVI. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XVII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XVIII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XIX. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XX. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XI. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XIII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XIV. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XV. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XVI. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XVII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XVIII. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XIX. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01
		XX. <i>Activity to find out which plant grows best in which soil</i>	10	26.11.23	80-01


Circuit diagram:

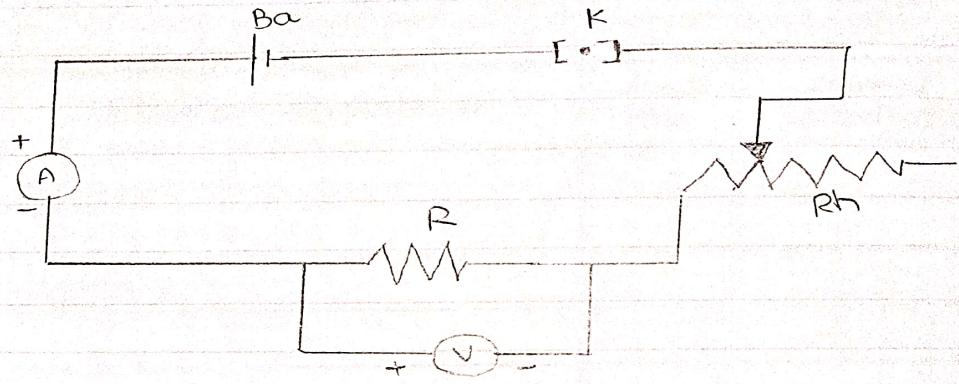

where :

Ba - Battery, K - Plug key, A - Ammeter, V - Voltmeter,
Rh - Rheostat, R - Resistance of given wire.

Nature of graph:

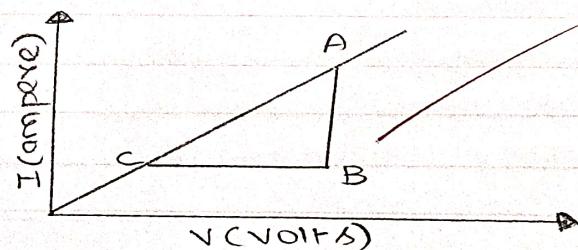

Date : 7.9.23

Expt. No. 1

Page No. 02

RESISTIVITY OF WIRES

AIM: To determine resistivity of a given wire by plotting a graph of potential difference versus current.

APPARATUS: Two wires of unknown resistance, battery eliminator (0 to 3V), voltmeter (0-5V), ammeter (0-5A), rheostat, plug key, connecting wires.

PRINCIPLE:

Ohm's law states that the electric current flowing through a conductor is directly proportional to the potential difference across its end, provided the physical state of the conductors remains unchanged.

FORMULA:

$$R = \frac{V}{I}$$

$$\text{Resistivity } \rho = \frac{RA}{L}$$

PROCEDURE:

- (1) Connect various components - resistance wire, rheostat, battery, key, voltmeter and ammeter as shown in circuit diagram.
- (2) Note whether pointers in ammeter and voltmeter coincide with zero mark on the measuring scale. If it is not so, adjust the pointer.

Observations:

$$\text{Radius of given wire } (r) = 1.33 \times 10^{-3} \text{ m}$$

$$\text{Length of the given wire } (l) = 40 \times 10^{-2} \text{ m}$$

S.No	Applied potential difference (V in volts)	current through the wire (I in ampere)
1.	0.1	0.15
2.	0.2	0.2
3.	0.3	0.25
4.	0.4	0.3
5.	0.5	0.35
6.	0.6	0.4

Radius of given wire (r) = $1.33 \times 10^{-3} \text{ m}$

$$\text{Length of the given wire } (l) = 40 \times 10^{-2} \text{ m}$$

S.No	Applied potential difference (V in volts)	current through the wire (I in ampere)
1.	0.1	0.7
2.	0.2	1.15
3.	0.3	1.65
4.	0.4	2.00

- (3) Insert the key K and slide the rheostat contact to one of its extreme ends, so that current passing through the resistance wire is minimum.
- (4) Note the ammeter and voltmeter readings.
- (5) Remove the key K and allow the wire to cool, if heated. Again insert the key. Shift the rheostat contact slightly to increase the applied voltage. Note the ammeter and voltmeter reading.
- (6) Repeat step 5 for five to six different settings of the rheostat. Record your observation in a tabular column.
- (7) Plot a graph between the potential difference across the wire (V) vs current (I).
- (8) The resistance of the given wire is equal to the reciprocal of the slope.
- (9) Resistivity can be calculated by given formulae.
- (10) We will repeat the procedure with one/two more wires.

RESULT: Resistivity of the given wires

$$\text{First wire} = 0.75 \Omega \quad 1.04 \times 10^{-5} \Omega \cdot \text{m}$$

$$\text{Second wire} = 0.66 \Omega \quad 0.92 \times 10^{-5} \Omega \cdot \text{m}$$

PRECAUTIONS:

- (1) The connections should be neat, clean and tight.
- (2) The rheostat should be moved smoothly.
- (3) Reading should be taken without any parallax error.

calculation: To find the resistance of wire with thickness

calculated length of 0.6 m and width of 0.3 m

First wire measured at 0.75 ohm so it is not discarded

From graph, slope = $\frac{AB}{BC} = \frac{0.4 \times 0.6}{0.6 \times 0.3} = \frac{0.24}{0.18}$ ohm

length of wire is given as 0.6 m so it is discarded

The resistance of the given wire is $R = \frac{0.1}{\text{slope}} = \frac{0.1}{1.33} = 0.75$ ohm

so it is discarded as it is longer than required

Second wire as length of 0.3 m is required

From graph, slope = $\frac{AB}{BC} = \frac{0.5 \times 0.3}{0.3 \times 1} = \frac{0.45}{0.3}$ ohm

The resistance of the given wire is $R = \frac{0.1}{\text{slope}} = \frac{0.1}{1.5} = 0.66$ ohm

so it is discarded as it is longer than required

so it is discarded as it is longer than required

so it is discarded as it is longer than required

so it is discarded as it is longer than required

so it is discarded as it is longer than required

so it is discarded as it is longer than required

so it is discarded as it is longer than required

CHART NO. 3.15

adopt due care and take care while drawing the chart

plotting the points and always take care that

values are marked on the chart and values are marked

Date

Expt. No.


Page No. 04

~~Source of error:~~

- (1) ~~Connections maybe loose.~~
(2) ~~The wire may not have uniform thickness.~~

~~d~~

Circuit Diagram:

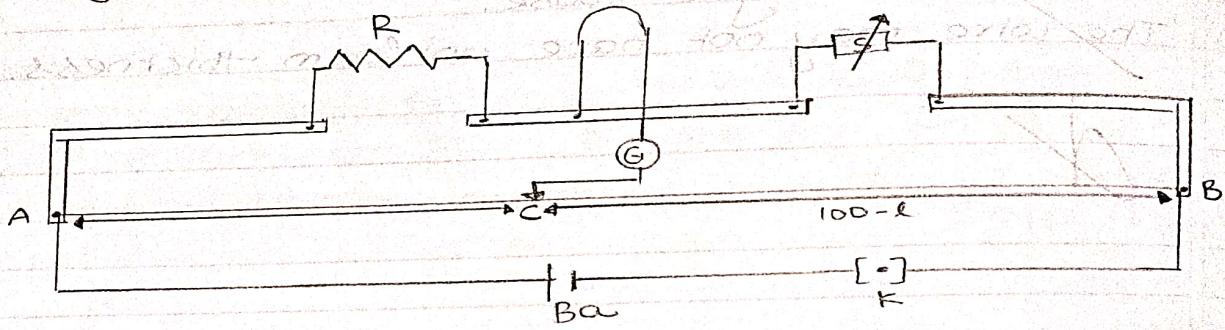

Where: AB - Meter bridge wire, Ba - Battery, K - Plug key,
S - Standard resistance box, R - Resistance of given wire,
C - Balancing point, G - Pointer galvanometer, AC - Balancing length

Date 21.9.23

Expt. No. 2

Page No. 05

METER-BRIDGE - RESISTANCE OF GIVEN WIRE

AIM: To determine the resistance of the given wire using meter bridge and hence determine the resistivity of the material of the wire.

APPARATUS: Meter Bridge, experimental wire, battery, plug key, resistance box, jockey and pointer galvanometer.

PRINCIPLE:

A meter bridge works on the principle of balanced wheatstone's bridge. The wheatstone bridge is said to be balanced when the current through the galvanometer is zero.

FORMULA:

Resistance of the wire

$$R = \frac{Sl}{100-l} r$$

where:

S - Standard resistance

l - Balancing length

L - Length of the experimental wire

r - Radius of the experimental wire.

Procedure:

- (1) The connections are made as shown in the circuit diagram.

Observations:

Length of the given wire (L) = 50 cm
 Radius of the given wire (r) = 0.133 cm

To measure the resistance of the given wire:

S. No.	Resistance R in ohms	Balancing length l in cm	$R = \frac{Sl}{100-l}$ in ohms
1.	0.1	90.3	0.93
2.	0.3	84.7	1.66
3.	0.5	79.9	1.987

$$R = \frac{Sl}{100-l} \text{ ohms}$$

Average value of resistance = 1.525 ohms

Series add to zero

$$0.1 + 0.3 + 0.5 = 1.00$$

Series add to zero

Date

Expt. No.

Page No... 06

- (2) A suitable resistance s is ^{un}plugged in the standard resistance box.
- (3) The circuit is checked for opposite deflections by placing jockey at the two ends of the wire AB alternatively.
- (4) The jockey is moved on the wire from the end A towards B till the galvanometer shows zero deflection.
- (5) The balancing length l is measured. The resistance of the wire is calculated using the formula
- $$R = \frac{sl}{100-l}$$
- (6) The experiment is repeated for different values of s and average value of R is found.
- (7) The length and radius of the experimental wire is measured using meter scale and screw gauge.

RESULT:

The resistance of the given wire is 1.525Ω

PRECAUTIONS:

- (1) The connections should be neat, clean and tight.
- (2) All the plugs in the resistance box should be tight.
- (3) Move the jockey gently over the bridge wire and do not rub it.
- (4) The plug in key K should be inserted only when the observation is to be taken.

Date

Expt. No.


Page No. 07

Source of error:

- (1) Connections may be loose.
(2) The wire may not have uniform thickness.

~~Q1~~

CIRCUIT DIAGRAM:

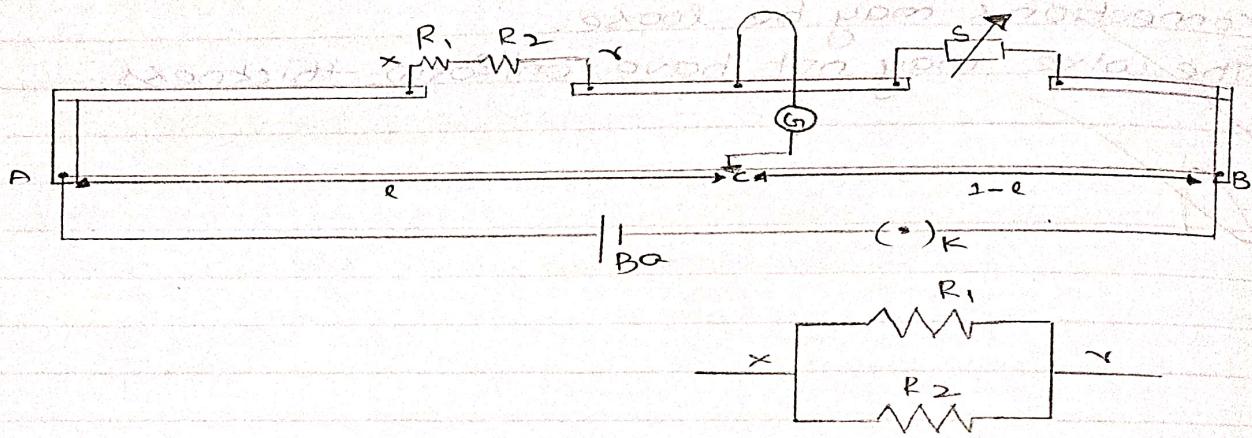

Where:

R_1 and R_2 - given resistors, S - standard resistance box,

G - galvanometer, Ba - Battery, K - plug key

AB - Meter Bridge wire

AC - Balancing length.

Date 5.10.23

Expt. No. 3

Page No. ... 08

METER BRIDGE - COMBINATION OF RESISTANCE

AIM: To verify the laws of combination of resistance in series and using meter bridge

APPARATUS: Meter bridge, battery, two resistors, plug key, resistance box, galvanometer and jockey.

PRINCIPLE:

The series or parallel combinations of two resistors are connected in the left gap of meter bridge R. A standard resistance S is connected in the right gap of the meter bridge. When the bridge is balanced the current through the galvanometer is zero, i.e. the jockey is at the point C. The balancing condition is,

EFFECTIVE RESISTANCE OF COMBINATION (R_S OR R_p) - Resistance of the

wire AC

Resistance of the
wire BC

$$= \frac{l}{100-l}, \quad (\because R \propto l)$$

The effective resistance of combination is given by

$$R_s \text{ or } R_p = S \left(\frac{l}{100-l} \right)$$

- (1) Resistance of given resistor, $R_1 = 2 \Omega$
 (2) Resistance of given resistor, $R_2 = 1 \Omega$

To verify the laws of combination of resistance in parallel circuit first series combination

S.No	Resistance s in Ω	Balancing length l in m	$R_S = \frac{Sl}{100-l}$ in Ω
1.	2	6.9	2.22
2.	2	5.9	2.87
3.	3	4.9	2.88

sat. bounded & spt. spt. rad/a = $\sqrt{R_s}$ mean $R_s = 2.65 \text{ -} 2$

calculations: added up all the values after 1800 and got 16 values

Theoretical, $R_S = R_1 + R_2$

$$P_S = \frac{2+1}{2+2} = \frac{3}{4}$$

201-30 530013429

DR. G. E. COOKE

$$\left(\frac{1}{x-0.01} \right)^2 = e^{-q_2 x} \approx 1$$

FORMULA :

$$\text{Resistance, } R = \frac{sl}{100-l} \quad \Omega$$

Equivalent resistance in series, $R_s = R_1 + R_2 \quad \Omega$
where :

s - Standard resistance

l - Balancing length

R_1 and R_2 - individual resistances.

PROCEDURE :

- (1) The connections are made as shown in the circuit diagram i.e., the two resistors are connected in series.
- (2) A suitable resistance s is unplugged in the standard resistance box.
- (3) The circuit is checked for opposite deflections by jockey at the two ends of the meter bridge wire AB alternately.
- (4) ~~The jockey is moved on the wire from the end A towards B till the galvanometer shows zero deflection.~~
- (5) The balancing length, is measured. The equivalent resistance of the series combination is calculated using the formula $R_s = \frac{sl}{100-l}$
- (6) The experiment is repeated for different value of s and average value of R_s is found. The theoretical value of equivalent resistance is calculated using the formula $R_s = R_1 + R_2$

- (7) Now the two resistors are connected in parallel on the left gap of meter bridge.
- (8) the jockey is moved on the wire and hence balancing length l is measured. The equivalent resistance of the parallel combination is calculated using the formula $R_g = \frac{sl}{100-l}$

RESULT:

Theoretical value of resistances in series, $R_s = 3\Omega$
 Experimental value of resistances in series, $R_s = 2.65\Omega$
 Experimental values are in good agreement with theoretical values, thus the laws of combination of resistances in series are verified.


PRECAUTIONS:

- (1) The connections should be neat, clean and tight
- (2) All the plugs in the resistance box should be tight.
- (3) Move the jockey gently over the bridge wire and do not rub it.
- (4) The plug in key K should be inserted only when the observation is to be taken.

~~**Source of error:**~~

- (1) Connections maybe loose.
- (2) the wire may not have uniform thickness.

Q1. ~~Diagram~~

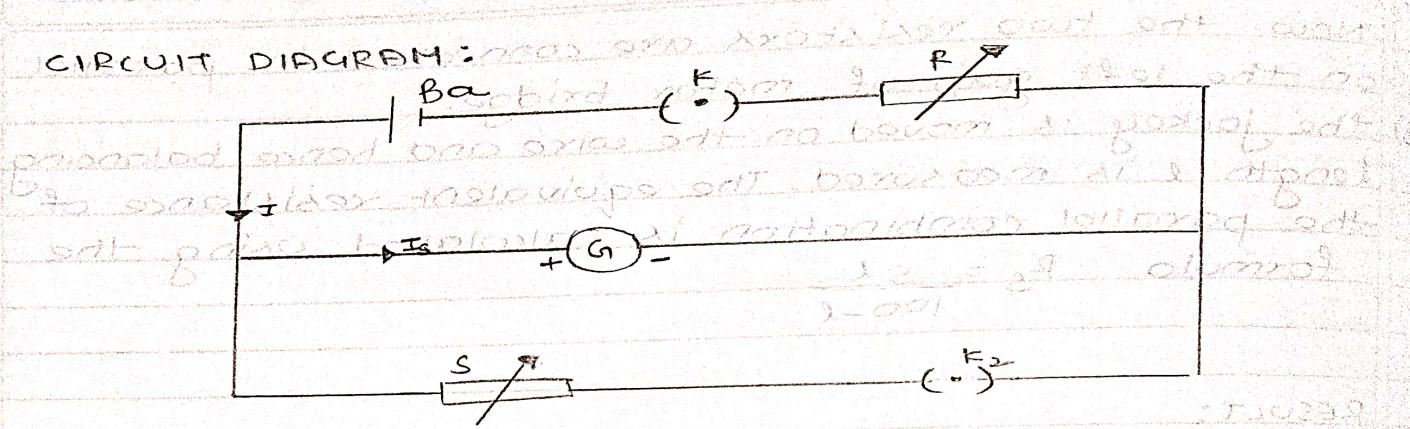

where:
Ba - Battery, G - Galvanometer, R - Resistor
K₁ and K₂ - plug keys are used to connect
to other add. For each add switch is connected
between the two sets of add.

object has also been added additional add.
object and bridge and series between the two add.
the two series object with two different add. add
the two objects are connected in parallel add.
the two objects are connected in parallel add.

object object add
add. object add

FIGURE OF MERIT

AIM: To determine resistance of galvanometer by half deflection method and to find its figure of merit.

APPARATUS: Galvanometer, battery, two resistance boxes, one way key (two numbers) and connecting wires.

THEORY: A galvanometer is a device used to detect small current in a circuit. It has a coil pivoted in a radical magnetic field. When electric circuit is passed through the coil, it gets deflected. Its deflection is noted by attaching a pointer to the coil. The deflection is proportional to current passed. A galvanometer has a moderate resistance and has a small current carrying capacity. The resistance of a galvanometer can be found by half deflection method. The circuit is shown for this method. Key K is inserted and deflection O is determined with a suitable value of R. If E is the emf of cell and I be the current in circuit, the galvanometer resistance

$$G = \frac{R_S}{R - S}$$

Figure of merit of galvanometer: It is defined as current required for producing deflection of 1 division. It is measured in ampere/div. When a high resistance R is taken out from resistance box, a current I flows in the circuit and it produces

Observation:

S.NO	Resistance Ω	Deflection in galvanometer (θ)	$\theta/12$ (divisions)	Shunt S Ω	Galvanometer Resistance $G\Omega$	Figure of merit $K = \frac{E}{R+G}$
1.	5000	15	120	8	121.82	1.53×10^{-5}
2.	5000	20	120	10	122.64	1.75×10^{-5}
3.	4650	30	120	15	123.17	1.39×10^{-5}
4.	5400	18	120	9	122.58	1.71×10^{-5}

$$\text{Mean } K = 1.7512 \times 10^{-5} \text{ A/division}$$

Estimated error in figure of merit is ± 0.000002 . Hence
 the experimental values obtained are as follows:
 1. $R = 5000 \Omega$, $G = 121.82 \Omega$, $K = 1.53 \times 10^{-5} \text{ A/division}$
 2. $R = 5000 \Omega$, $G = 122.64 \Omega$, $K = 1.75 \times 10^{-5} \text{ A/division}$
 3. $R = 4650 \Omega$, $G = 123.17 \Omega$, $K = 1.39 \times 10^{-5} \text{ A/division}$
 4. $R = 5400 \Omega$, $G = 122.58 \Omega$, $K = 1.71 \times 10^{-5} \text{ A/division}$

$$29 - 23 \\ 2 - 9$$

2. In this part, the resistance of the galvanometer is to be measured.
 To do this, the potentiometer is connected in series with the galvanometer and the current through the circuit is to be measured by the ammeter. The galvanometer is connected in parallel with the ammeter. The total current flowing through the galvanometer and the ammeter is to be measured by the ammeter. The galvanometer is connected in parallel with the ammeter. The total current flowing through the galvanometer and the ammeter is to be measured by the ammeter.

a deflection θ .

Therefore, $T = \frac{E}{R+G} = k\theta$

$$\frac{E}{(R+G)\theta}$$

By varying R and noting corresponding value of θ , we can find a set of values of figure of merit. The mean of these values gives the figure of merit.


PROCEDURE:

- Make the connections as shown.
- See that the plug of resistance box are tight.
- Introduce a resistance of 5000 from the resistance box R and then insert the key K only.
- Adjust the value of R so that the deflection in the galvanometer is maximum (say 30 div)
- Note the deflection. Let it be θ i.e., $\theta = 30$ div
- Now, insert the key K_2 without changing the value of R, adjust the value of K, such that deflection in galvanometer reduces exactly to half the value obtained i.e., $\theta/2$.
- Note the value of R.
- Repeat the above steps for various values of R.

RESULT:

- The resistance of galvanometer is found to be
- Figure of merit of galvanometer is 1.512×10^{-5} A/division

DIAGRAM

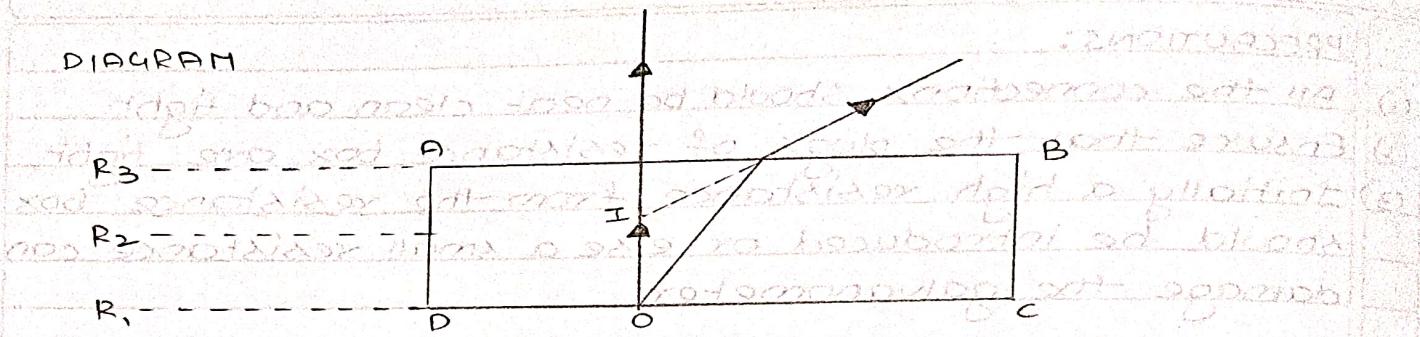

where:

ABCD - Rectangular glass slab, O - Object, I - Image

R_3 - position of particles on glass slab,

R_2 - position of image (object seen through glass slab)

R_1 - position of object.

Date 8.11.23

Expt. No. 5

Page No. 14

REFRACTIVE INDEX OF GLASS

AIM: To determine the refractive index of glass using travelling microscope.

APPARATUS: Travelling microscope, a glass slab, chalk dust and paper.

PRINCIPLE: If a glass slab is placed in air or horizontal surface and its bottom surface is viewed from top, it appears to be elevated due to the refraction. The distance between the apparent bottom and the top surface of the slab gives the apparent thickness of the slab. In case of normal observation, the refractive index of the glass with respect to air is the ratio of real thickness of glass slab to the apparent thickness.

FORMULA:

(1) Total reading $TR = MSR + (CVD \times LC) \text{ cm}$

(2) Refractive index of glass slab $n_g = \frac{R_3 - R_1}{R_3 - R_2}$

where: MSR - Main scale reading.

CVD - coincide vernier scale division.

LC - Least count

R_1 - travelling microscope reading when focussed on object (ink mark) through air.

R_2 - travelling microscope reading when focussed

Observations:

The value of IMSD of travelling microscope (s) = 0.05 cm
 Total number of VSD (N) = 50
 Least count (LC) = The value of IMSD = $\frac{0.05}{50} = 0.001 \text{ cm}$

S.NO	Travelling microscope Reading for											
	Mark made on paper	Mark made on paper through glass slab	Particles on the top of glass surface		MSR	CVD	TR in cm (CR ₁)	MSR	CVD	TR in cm (CR ₂)	MSR	CVD
in cm	in div	in cm	in div	in cm	in div	in cm	in div	in cm	in div	in cm	in div	in cm
1-2	3.2	4.5	3.6	4.2	3.7	4.5	5.7	4.4	6.1			

Refractive index of the slab (n_g) = $\frac{\text{Real thickness of the slab}}{\text{Apparent thickness of the slab}}$

$$\frac{R_3 - R_1}{R_3 + R_1 - 2R_2} = \frac{n_g - 1}{n_g + 1}$$

$$= \frac{6.1 - 3.6}{6.1 + 3.6 - 2 \times 4.5} = \frac{2.5}{1.6} = 1.5$$

$$= \frac{6.1 - 4.5}{6.1 + 4.5 - 2 \times 3.6} = \frac{1.6}{9.2} = 0.17$$

Refractive index of air (n_a) = $\frac{1}{\sin i / \sin r} = \frac{1}{\sin 45^\circ / \sin 60^\circ} = 1.5$

Refractive index of glass (n_g) = $\frac{n_g - 1}{n_g + 1} = 1.5$

Date _____

Expt. No. _____

Page No. 15

on image when glass slab is kept on object

R_3 - travelling microscope reading when focussed on the particles on the surface of glass slab.

PROCEDURE :

- (1) The least count of travelling microscope is calculated.
- (2) A sheet of white paper with ink mark is placed on the base of travelling microscope.
- (3) The microscope is adjusted to focus on the ink mark on the paper and readings are noted in vertical scale and total reading (R_1) is found using relevant formula.
- (4) Now glass slab is placed on the paper and the microscope is focussed on the ink mark through glass slab and corresponding reading R_2 is found.
- (5) Some chalk dust is sprinkled on the upper surface of the glass slab the microscope is focussed on chalk dust and corresponding reading R_3 is found.
- (6) Refractive index of glass slab is calculated using the formula $n_g = \frac{R_3 - R_1}{R_3 - R_2}$
- (7) The experiment is repeated for one more trial to raise the position of glass slab and hence calculated the refractive index. Then mean refractive index is found.

RESULT: The refractive index of glass is $(n_g) = 1.5$

Date

Expt. No.

Page No. 16

PRECAUTIONS:

- (1) In microscope, the parallax should be properly removed.
- (2) the microscope should be moved in upper direction only to avoid back lash error.

Sources of error:

- (1) The microscope scale may not be properly calibrated.

~~d~~

DIAGRAM:

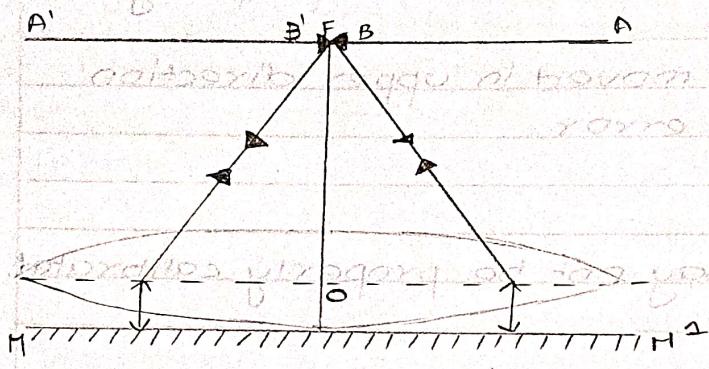


Figure - 1

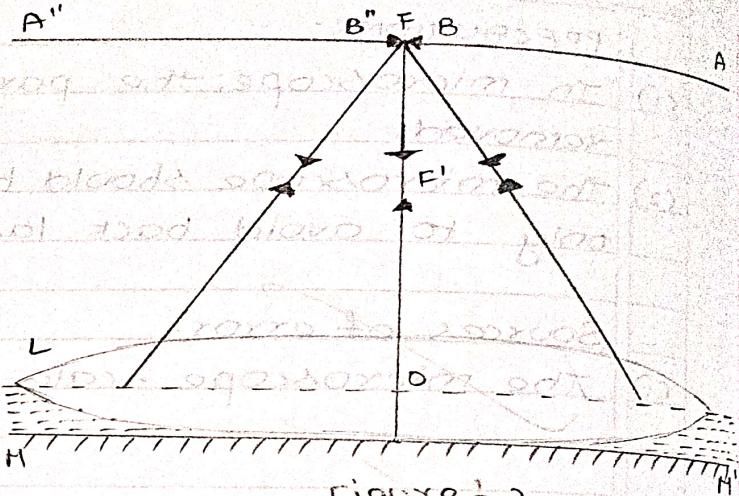


Figure - 2

Where:

L - convex lens, MM' - plane mirror, AB - object pin, A'B' - image by convex lens, O - optic centre, A''B'' - image by combination of water lens and convex lens.

Date 22-11-23

Expt. No. 6

Page No. ... 17

REFRACTIVE INDEX OF WATER BY CONVEX LENS.

AIM: To determine the refractive index of water using convex lens and plane mirror.

APPARATUS: Plane mirror, convex lens, laboratory stand with rigid base and clamp arrangement, water, a pin, a plumb line, spherometer and a meter scale.

PRINCIPLE: The reciprocal of the equivalent focal length of the combination of the lens is the equal to the sum of the reciprocal of focal lengths of individual lenses.

In Figure - 1, $OF - F$ is the focal length of the convex lens. In Figure - 2, $OF' - F'$ is the equivalent focal length of combination of convex lens and the plane-concave lens of water. If F_w is the focal length of the plane-concave lens of water.

$$\frac{1}{F'} = \frac{1}{F} + \frac{1}{F_w}$$

$$\frac{1}{F_w} = \frac{1}{F'} - \frac{1}{F}$$

$$\therefore F_w = \frac{FF'}{F - F'}$$

From lens maker's formula the focal length of plane-concave water lens,

$$\frac{1}{F_w} = (n_w - 1) \left(\frac{1}{r} \right) \text{ where } F_w - \text{magnitude of the}$$

OBSERVATIONS

(i) The radius of curvature of the given convex lens (R) =
 To measure the focal length of water lens:

S.No	Position of pin with respect to the optical center O			Distance of pin with water from upper surface of the lensed mirror (d ₂ ', cm)			$F_w = \frac{FF'}{F-F'}$ in cm
	Upper surface of lens (d ₁ , cm)	Plane	$F = \frac{d_1+d_2}{2}$ in cm	upper surface of the lensed mirror (d ₂ ', cm)	Plane	$F' = \frac{d_1+d_2'}{2}$ in cm	
1.	20.8	21.1	21.1	30.6	31.2	36.9	66.5

$$\text{Mean } F_w = 66.5 \text{ cm}$$

Calculation:
 Focal length of the plane-concave lens of water
 ~~$F_w = \frac{FF'}{F-F'}$~~
 ~~$F = F'$~~
 ~~$F_w = \frac{FF'}{F-F'}$~~
 ~~$F = F'$~~
 ~~$F_w = \frac{FF'}{F-F'}$~~
 Refractive index of water $\frac{F_w}{F_{\text{air}}} = \frac{F_w}{F} = \frac{66.5}{20} = 3.32$

$$\frac{1}{n} = 1 + \frac{100}{665} = 1.32$$

and the refractive index of water is more than that of air

Expt. No.

Date

Page No. 18

Focal length of plano-convex concave water lens

$$n_w = \frac{1 + R}{|F_w|}$$

FORMULA:

(1) Focal length of plano-concave water lens $F_w = \frac{FF'}{F - F'}$ (2) Refractive index of water, $n_w = \frac{1 + R}{F_w}$

where: F - Focal length of convex lens

F' - Equivalent focal length of combination of convex lens and plano-concave water lens.

PROCEDURE:

- (1) A plane mirror is placed on the base of laboratory stand keeping its reflecting surface upward.
- (2) A convex lens is placed on the plane mirror as shown in figure.
- (3) A sharp edged bright pin AB is placed horizontally just above the optic center (O) of the convex lens and clamped.
- (4) The position of the pin AB' is adjusted such that it coincides with its image A'B' without parallax.
- (5) The vertical distance between the optic center (O) of convex lens and pin is measured using plumb line. It's equal to the focal length F of convex lens.
- (6) A few drops of water are put under the lens with the help of syringe so that the space between the mirror and lens is filled with water.

Date

Expt. No.

Page No. ... 19

- (7) The position of the pin AB is raised such that it coincides with its image A "B" without parallax.
- (8) Then vertical distance between the optic center (O) of convex lens and pin AB is measured by plumb line, which is equal to the effective focal length f' of the combination lens and water lens.
- (9) The focal length of water lens is calculated using the relevant formula.
- (10) The radius of curvature of the spherical surface of the convex lens in contact with water is found by using spherometer.
- (ii) Refractive index of water is calculated using the formula.

PRECAUTIONS:

- (1) The parallax should not be there.
- (2) Meter scale should be straight while taking reading.
- (3) Air bubbles should not be there in water.

Sources of error:

- (1) Formation of air bubbles in water.
- (2) ~~Impurities in water.~~

~~A~~

Date 9.11.23

Expt. No. 7

Page No. 20....

ANGLE OF MINIMUM DEVIATION

AIM: To determine the angle of minimum deviation for a given glass prism by plotting graph between angle of incidence and the angle of deviation.

APPARATUS: Drawing board, prism, drawing pins and white paper.

PRINCIPLE:

A ray of light incident on one of the refracting surface of prism of angle A and refractive index n , it will deviate while passing through prism as shown in figure- 1. The deviation is given by $d = (i_2 + l_2) - A$ where i_2 and l_2 are angle of incidence and angle of emergence.

As the angle of incidence is gradually increased, the angle of deviation first decreases reaches a minimum value (d_m) and then increases as shown in graph. When the angle of incidence is equal to the angle of emergence, the deviation is minimum.

PROCEDURE:

- (1) A straight line X_4 is drawn on the sheet of white paper fixed on the drawing board.
- (2) The points O_1, O_2, O_3, \dots are marked on line X_4 .
- (3) The normal $N_1 O_1$ is drawn to X_4 at O_1 and straight line OO_1 is drawn to represent ray of incidence

Observations:

S. No	Angle of incidence	Angle of deviation
1	30°	45°
2	35°	41°
3	40°	40°
4	45°	40°
5	48°	40°
6	55°	43°
7	60°	45°

A refracted ray has an angle of deviation which is measured by the angle between the incident ray and the refracted ray.

Calculation: If μ is refractive index of glass and θ_i is angle of incidence, then angle of deviation $\theta_d = \mu \sin(\frac{\theta_i}{2})$.

Consider a prism of refractive index μ with angle B . If θ_i is angle of incidence, then angle of deviation $\theta_d = \mu \sin(\frac{\theta_i}{2})$. If $\theta_i = 60^\circ$, then $\theta_d = \mu \sin(30^\circ) = \mu/2$. If $\mu = 1.5$, then $\theta_d = 75^\circ$.

which makes an angle 45° with N.O.

- (4) The prism ABC is placed on the paper as shown in the figure and its boundary is drawn.
- (5) Two pins P, and Q, are vertically fixed about 5cm apart on the ray of incidence D.O.
- (6) While seeing the images of the pins P, and Q, through the other refracting surface BC of the prism, two more pins R, and S, are fixed on the side of AC so that R,S, and the images of the pins P, and Q, will be collinear.
- (7) Pins are removed and their pricks are marked. A straight line is drawn through the pin pricks of R, and S, to obtain the ray of emergence.
- (8) The ray of incidence and emergence are extended as shown in the figure - 2 to find the angle of deviation (d)
- (9) The experiment is repeated for different value of angle of incidence and to find the corresponding angle of deviation.
- (10) A graph of angle of incidence (i) versus angle of deviation (d) is drawn and angle of minimum deviation d_m is found from the graph.

~~RESULT:~~ The angle of minimum deviation, $d_m = 40^\circ$

PRECAUTIONS:

- (1) The angle of incidence should lie between $35^\circ - 60^\circ$
- (2) The pins should be fixed vertically.

Date

Expt. No.

Page No. 22


- (3) The distance between the two pins should not be less than 10mm.
- (4) Arrow heads should be marked to represent incident and emergent rays.
- (5) The same angle of prism should be used for all observations.

~~Sources of error:~~

- (1) Pin pricks may be thick.
- (2) Measurement of angles may be wrong.

~~A~~

CIRCUIT DIAGRAM:

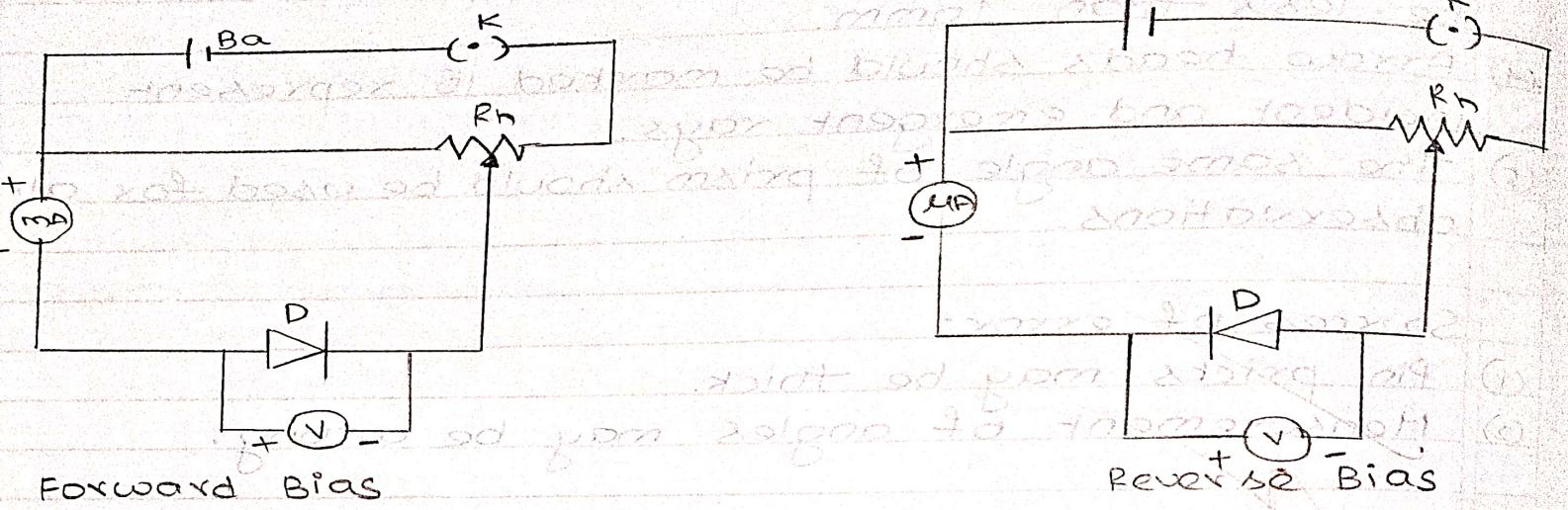


Forward Bias

Reverse Bias


where:

B_a - Battery, V - Voltmeter, mA - Micro ammeter, mA - Milli ammeter, R_h - Rheostat, D - Diode, K - plug key

Nature of Graph:

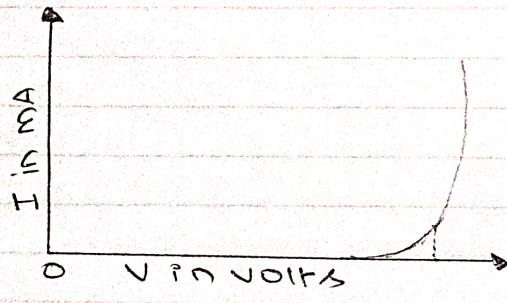

FORWARD BIAS

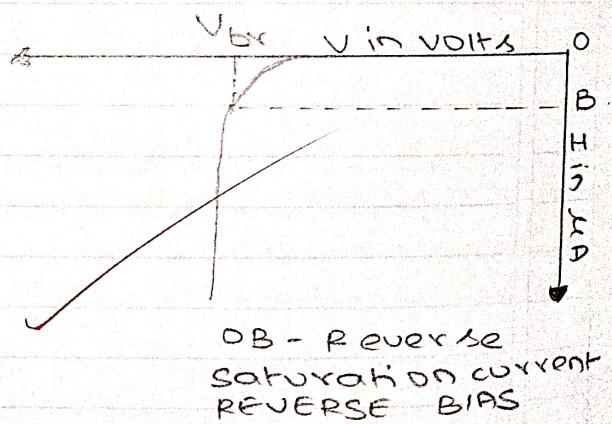

V_{BR} - Reverse saturation current
REVERSE BIAS

SEMI-CONDUCTOR DIODE

AIM: To draw the I-V characteristic curve of a P-N junction in forward bias and reverse bias.

APPARATUS: A p-n junction diode, milliammeter, microammeter, voltmeter, rheostat and battery.

PRINCIPLE: When p-side of the semi-conductor diode is connected to the positive terminal of the battery, then p-n junction is said to be forward biased. The junction offers low resistance and initially a negligibly small current flows through circuit till the applied voltage crosses a certain value the diode current increases exponentially.

When p-side of the semi-conductor diode is connected to the negative terminal of the battery, then p-n junction is said to be reverse biased. As the applied voltage is increased in the reverse biased condition starting from zero, the current increases, but soon becomes constant. It is called reverse saturation current.

PROCEDURE:

- For forward bias:
The connections are made as shown in the circuit diagram.

OBSERVATIONS:

Forward bias characteristics		Reverse bias characteristics		
S.NO	voltage (v) in volts	current I in mA	SNO	
			Voltage (v) in volts	
1	0.06	600	1	0
2	0.02	0	2	5
3	0.04	0	3	10
4	0.60	0.5	4	15
5	0.66	2	5	20
6	0.72	7	6	25
7	0.68	4	7	30
8	0.62	1	8	35
			9	40

- (2) Using rheostat, the voltage is adjusted for a value V . The voltage V and corresponding current I are noted.
- (3) The voltage is increased in small steps. Value of V and I are noted in each case and readings are tabulated.
- (4) A graph is plotted for the current I versus voltage V .
- (5) Cut in voltage is located in the graph.
- (6) For reverse bias:
- (1) The connections are shown in the circuit diagram.
 - (2) Using rheostat, the voltage is adjusted for a value V . The voltage V and I are noted.
 - (3) The voltage is increased in small steps. Value of V and I are noted in each case and readings are tabulated.
 - (4) A graph is plotted for the current I versus voltage V .
 - (5) Reverse saturation current is found.

RESULT:

I-V characteristics of p-n junction diode are drawn.
 From graph: cut in voltage = $0P = 1.5V$
 cut out voltage = $0.6V$

PRECAUTIONS:

- (1) The connections should be neat, clean and tight.
- (2) Forward-bias voltage beyond breakdown should

Date -----

Expt. No. -----


Page No. 25

not be applied.

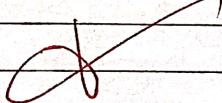(3) Reverse-bias voltage beyond breakdown should not be applied.


~~Source of error:~~

~~the junction diode applied may be faulty.~~




CIRCUIT DIAGRAM:

Diagram showing three bulb positions connected in parallel across a power source.

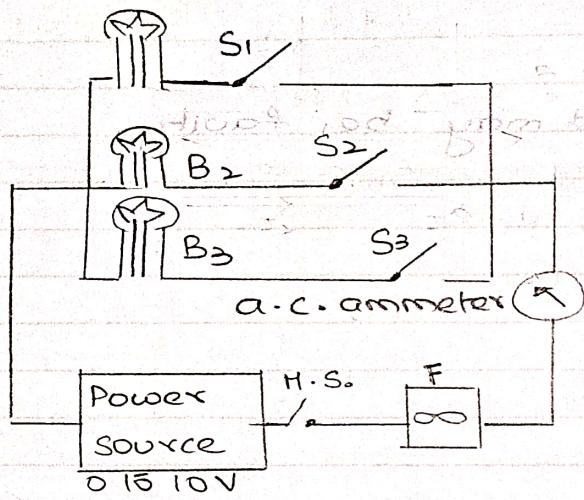

(a) Circuit diagram

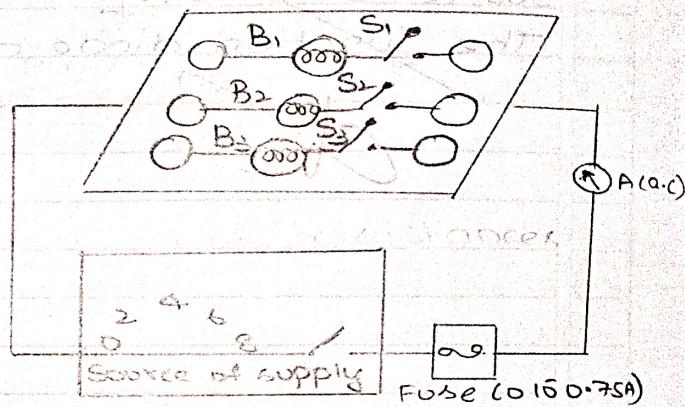

(b) Actual layout

SECTION - A

ACTIVITY - I

AIM: To assemble a household circuit, comprising three bulbs, three (on/off) switches, a fuse and a power source.

APPARATUS: No apparatus required in assembling a circuit.

MATERIAL: Three bulbs (6V, 1W) each, a fuse of 0.6A, main switch a power supply (battery eliminator), three (on/off) switches flexible connecting wire with red and black plastic covering, a fuse wire.

SUPPLEMENTARY: Main electric board with a two-pin socket and main switch.

THEORY:

Electricity supplied to us for domestic purposes is 220V a.c and 50Hz. The household circuit, all appliances are connected in "parallel" with mains. The switches are connected in series with each appliance in live wire. 5A switches are required for normal appliances like, bulbs, fluorescent tubes fans etc, 15A sockets and switches are required for heavy load appliances like, refrigerator, air conditioner, geyser, hot plates etc. All appliances must have three wires called live, neutral and the earth. Total power consumption 'P' at a time

$$P = P_1 + P_2 + P_3 \dots$$

Date 19/7/23

Expt. No.

Page No. 27


where P_1, P_2, P_3 are the powers drawn by appliances.
To protect the appliances from damage when unduly high currents are drawn fuse of little higher rating, 10 to 15 to 20% higher than the current normally drawn by all appliances. For further safety, a suitable value MAINS FUSE like rating 32A is connected in series with supply source.

PROCEDURE:

- (1) Connect the bulbs B_1, B_2 , and B_3 in series with switches S_1, S_2 and S_3 respectively and connect each set $B-S$. Connect main supply to a step-down transformer (battery eliminator) to get required voltage from 0 to 10V (0, 2, 4, 6, 8 and 10V)
- (2) Connect the mains fuse M-S. in series with the power supply (battery eliminator).
- (3) Connect an a.c. ammeter in series with the $B-S$ set.
- (4) Connect one end of power supply to one end of $B-S$ set.
- (5) Check the circuit once again to ensure that household circuit is complete.
- (6) Gradually increase the current to 0.75A, the fuse must burn off at about 0.6A.



CIRCUIT DIAGRAM:

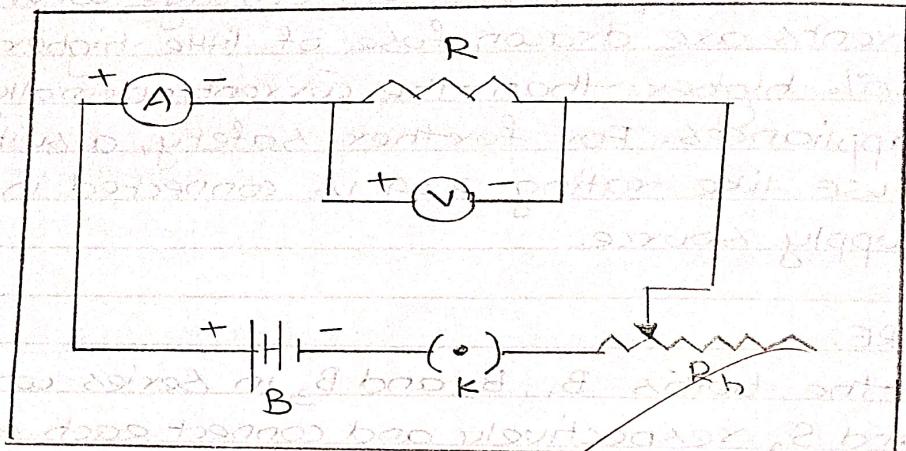

ACTIVITY- 2

PIN: To assemble the components of a given electrical circuit (Say Ohm's law circuit)

APPARATUS: A voltmeter and an ammeter of appropriate range, a battery, a rheostat, one way key.

MATERIAL: An unknown resistance or resistance coil, connecting wires, a piece of sand paper.

PROCEDURE:



- (1) Connect the rheostat in series with the battery with a key.
- (2) Connect the ammeter in series with the circuit, to measure the current.
- (3) Connect the voltmeter in parallel to the resistor, to measure the potential difference.
- (4) Connect the switch in series with the battery.
- (5) Assembly of the electrical components in electric circuit is complete. Connect the items as shown in the figure.

UTILITY:

It is used for measuring an unknown resistance.



CIRCUIT DIAGRAM:

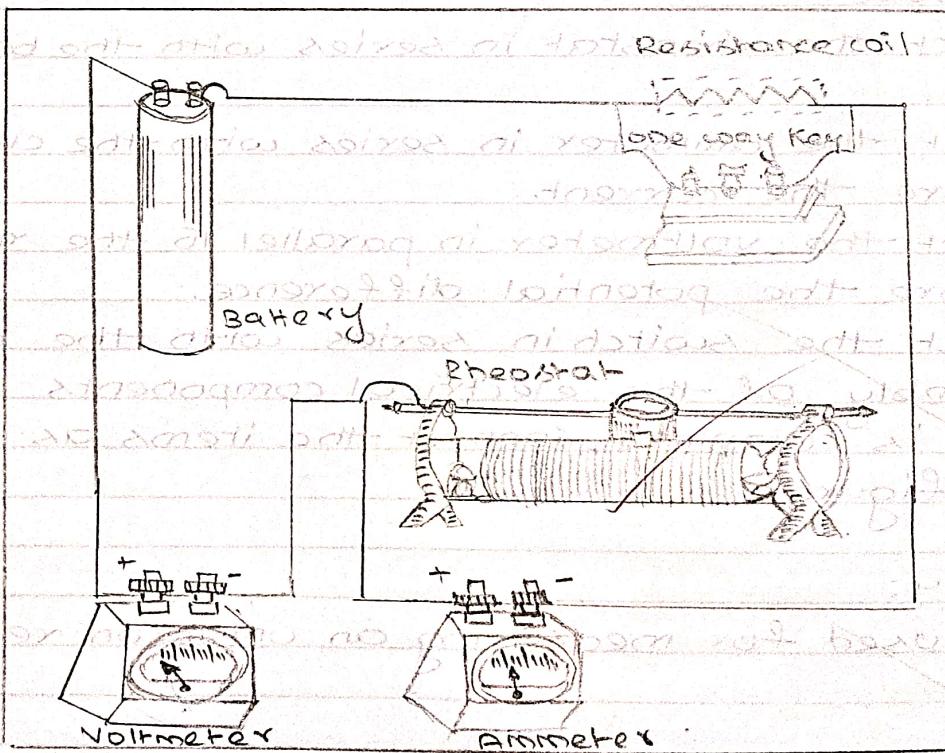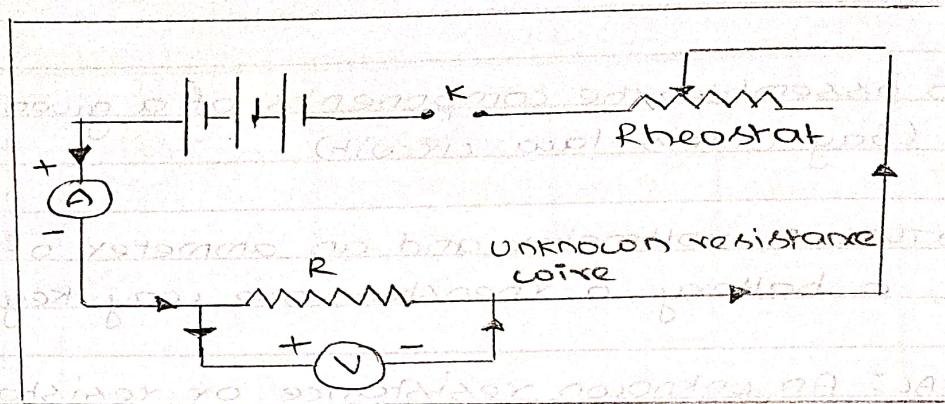

ACTIVITY-3

AIM: To draw the diagram of a given open circuit comprising at least a battery, resistor/rheostat, key, ammeter and voltmeter. Mark the components that are not connected in proper order and correct the circuit and also the circuit diagrams.

APPARATUS AND MATERIAL: A battery eliminator or a battery (0.15-6V), rheostat, resistance box (0.15-100Ω), two or one way key, d.c. ammeter (0-3)A and a d.c. voltmeter (0-3)V.

THEORY:

An open circuit is the combination of primary components of electric circuit in such a manner that on closing the circuit no current is drawn from the battery.

PROCEDURE:

~~Ammeter.~~ It should be connected in series with the battery eliminator.

~~Voltmeter.~~ It should be connected in parallel to resistor.

~~Rheostat.~~ It should be connected in series (in place of resistance coil) with the battery eliminator.


~~Resistance coil.~~ It should be connected in parallel (in place of rheostat).

~~One way key.~~ It should be connected in series to the battery eliminator.


Correct circuit diagram (components connected in proper order).

Electronic Components


Resistors

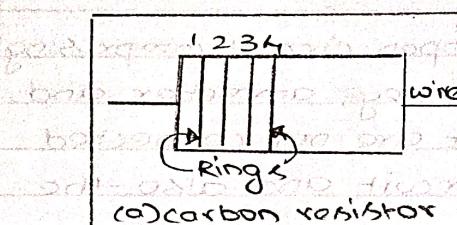


(a) carbon resistor

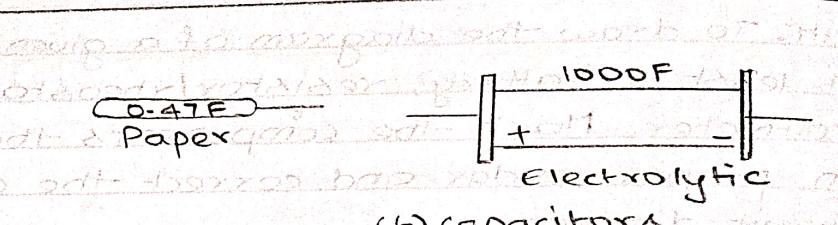


(b) capacitors

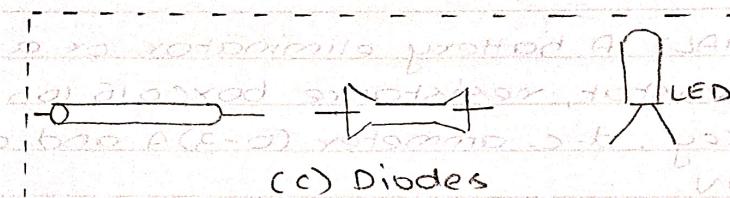

(c) Diodes

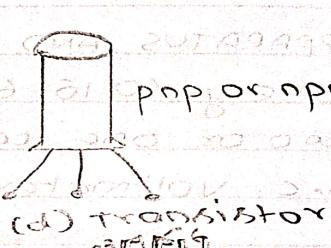

(d) transistor

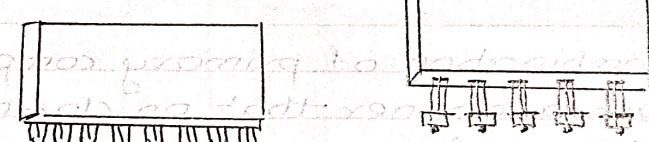

(e) integrated circuits

Some of the commonly available circuits

Diodes, resistors, capacitors and transistors are the most common electronic components used.

Resistor, diodes, capacitors and transistors are the basic components of electronic circuits.

Resistors are used to limit current flow in a circuit. They are also used to provide heat energy.

Diodes are used to rectify alternating current. This means they allow current to flow in one direction only.

Transistors are used to control current flow in a circuit. They are also used to amplify signals.

Capacitors are used to store electrical energy. They are also used to filter signals.

SECTION - B

ACTIVITY - 4

AIM: To identify a diode, an LED, a transistor, an IC, a resistor and a capacitor from a mixed collection of such items.

APPARATUS: Multimeter

MATERIAL: Above mixed collection of items.

THEORY:

For identification, appearance and working of each item will have to be considered.

- (1) A diode is a two terminal device. It conducts when forward biased and does not conduct when reverse biased. It does not emit light while conducting. Hence, it does not glow.
- (2) A LED (light emitting diode) is also a two terminal device. It also conducts when forward biased and does not conduct when reverse biased. It emits light while conducting. Hence, it glows.
- (3) ~~A transistor is a three terminal device. The terminals represent emitter (E), base (B) and collector (C).~~
- (4) ~~An IC (integrated circuit) is a multi-terminal device in form of a chip.~~
- (5) A resistor is a two terminal device. It conducts when either forward biased or reverse biased. (In fact there is no forward or reverse bias for a resistor). It conducts even when operated with A.C

OBSERVATIONS:

8 - 10 min

H - PRACTICAL

No. of obs	Number of legs	Name of device	No. of obs	Possible current flow through	Name of device
1.	More than 3	IC	4.	Unidirectional emit no light	Diode
2.	Three	Transistor	5.	Unidirectional emit light	LED
3.	Two	capacitor, diode LED or resistor	6.	Both direction (steady)	Resistor
			7.	Initial high but decays to zero	capacitor

OR D.C. voltage.

(4) A capacitor is also a two terminal device. It does not conduct when either forward biased or reverse biased. When a capacitor is connected to a d.c. source, then multi-meter shows some current initially but it decays to zero quickly. It is because that initially a capacitor draws a charge.

The components to be identified are shown in figure.

PROCEDURE:

- (1) If the item has four or more terminals and has form of a chip, it is an IC (integrated circuit).
- (2) If the item has three terminals, it is a transistor.
- (3) If the item has two terminals, it may be a diode, a LED, a resistor or a capacitor. To differentiate proceed as ahead.
- (4) Put the selector on resistance R of multimeter for checking continuity. The probe metal ends are inserted in terminal marked on the multimeter as common and P (or +ve). If such that the black one is in common and red probe is in P (or +ve). On touching the two ends of the device to the two other metal ends of probes.
 - (1) If pointer moves when voltage is applied in one way and does not move when reversed and there is no light emission, then item is a diode.
 - (2) If pointer moves when voltage is applied in one way and does not move when reversed and there is light emission, the item is a LED.
 - (3) If pointer moves when voltage is applied in one way and also when reversed, the item is a resistor.


Date

Expt. No.

Page No. 32

(a)

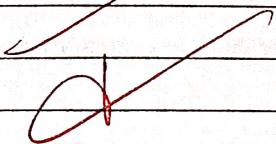If pointer does not move when voltage is applied in one way and also when reversed, the item is a capacitor.



ACTIVITY-5

AIM: To observe diffraction of light due to a thin slit between sharp edges of razor blades.

APPARATUS: Two razor blades, adhesive tapes, a screen, a source of monochromatic light (laser pencil) black and a glass plate.

THEORY:

Diffraction is a phenomenon of bending of light around the corners or edges of a fine opening or aperture.

Diffraction takes place when order of wavelength is comparable or small to the size of slit or aperture.

The diffraction effect is more pronounced if the size of the aperture or the obstacle is of the order of wavelength of the waves. The diffraction pattern arises due to interference of light waves from different symmetrical point of the same wavefront. The diffraction pattern due to a single slit consists of a central bright band having alternate dark and weak bands of decreasing intensity on both sides.


$$\text{For diffraction, } d \sin \theta = n\lambda$$

Here d = size of aperture or slit

θ = angle of diffraction

n = order of diffraction.

λ = wavelength of light

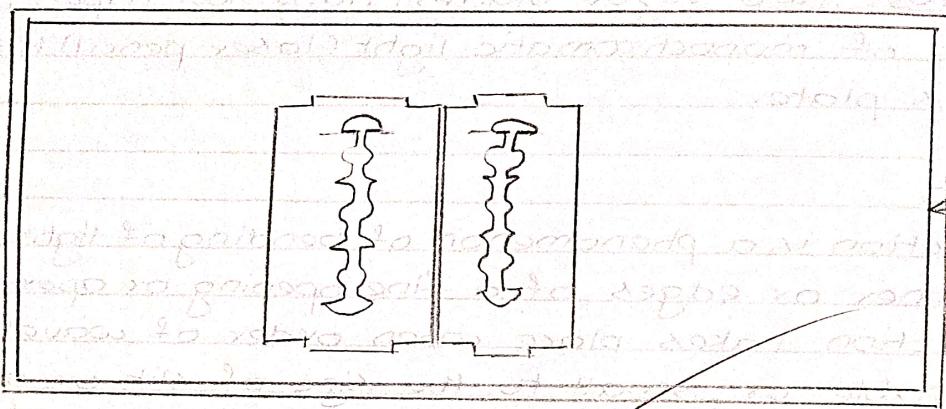

— Glass plate

Black paper

PROCEDURE:

- (1) Fix the black paper on the glass plate by using adhesive.
- (2) Place two razor blades so that their sharp edges are parallel and extremely close to each other to form a narrow slit in between, as shown in figure.
- (3) Cut the small slit in between the edges of blades and place at a suitable distance from a wall or screen of a dark room.
- (4) Throw a beam of light on the slit by the laser pencil.
- (5) A diffraction pattern of alternate bright and dark bands is seen on the wall.

CONCLUSION:

When light waves are incident on a slit or aperture then it bends away (spread) at the corners of slit showing the phenomena of diffraction of light.

PREDICTIONS:

- (1) Air gap should not be left between glass plates and black paper.
- (2) The razor blades should be placed extremely closed as possible.
- (3) Diffraction pattern should be seen on a wall of a dark room.
- (4) A point source of monochromatic light like laser torch should be used.

Expt. No.

Date 26.11.23

Page No. 35....

ACTIVITY 6

AIM: To study the nature and size of the image formed by a concave mirror on a screen by using a candle and a screen (for different distances of the candle from the mirror).

APPARATUS: An optical bench with three uprights, a concave mirror with holder, a burning candle, a card-board screen.

THEORY:

$$\text{From mirror formula } \frac{1}{v} + \frac{1}{u} = \frac{1}{f}$$

When $u = \infty$ (infinite), $v = -f$

when $u = -2f$, $v = -2f$

when $u = -f$, $v = \infty$ (infinite)

when $u < (-f)$, u becomes positive, image is virtual

Hence as the object (burning candle) is moved from infinity towards the concave mirror, its image (position of screen) moves from mirror focus towards infinity. The two cross each other at distance $2f$ i.e., at the centre of curvature of the mirror.

For candle distance less than focal length, image becomes virtual and does not come on screen.

PROCEDURE:

Find rough focal length of the concave mirror by usual method.

Mount the concave mirror in holder in first upright and keep it near one end of the optical bench, keeping mirror face inward.

Mount the card-board screen on a second upright and keep it at a distance equal 10 length of mirror, from first upright.

Mount the burning candle in third upright and keep it near other end of the optical bench.

Adjust heights so that the inverted image of erect flame of burning candle is formed on screen. Now the screen has to make the image sharp. The screen will be nearly at the focus of the concave mirror. The image will be real, inverted and much more diminished.

As the burning candle is moved towards the mirror, the screen has to be moved away from it for getting a sharp flame image. The inverted image size increases.

When the position of the candle approaches centre of curvature of the mirror, the screen also approaches the same position. The image size will be equal to the actual flame size.

Now interchange the uprights. Bring candle upright nearer to mirror than the screen upright.

Move the candle further nearer. The screen has to be moved away for getting an enlarged inverted real image on screen.

As the candle reaches the focus of the mirror, the screen may not be able to get its image.

Date

Expt. No.

Page No. ... 37

which will be formed at infinity i.e. beyond the length of the optical bench.

CONCLUSION:



This change in position, nature and size of the image is according to theoretical predictions.

~~DATA~~


Experiment No. :

RESISTIVITY OF WIRES

Date :

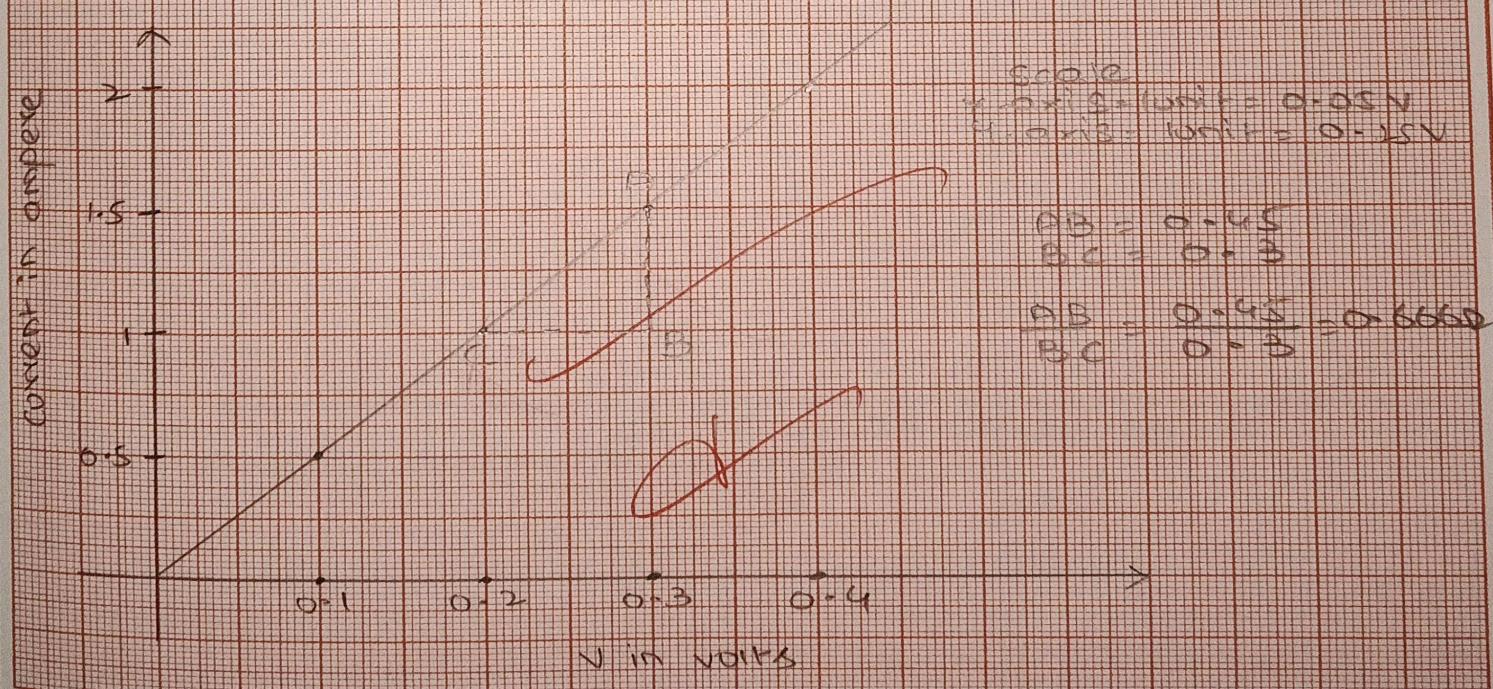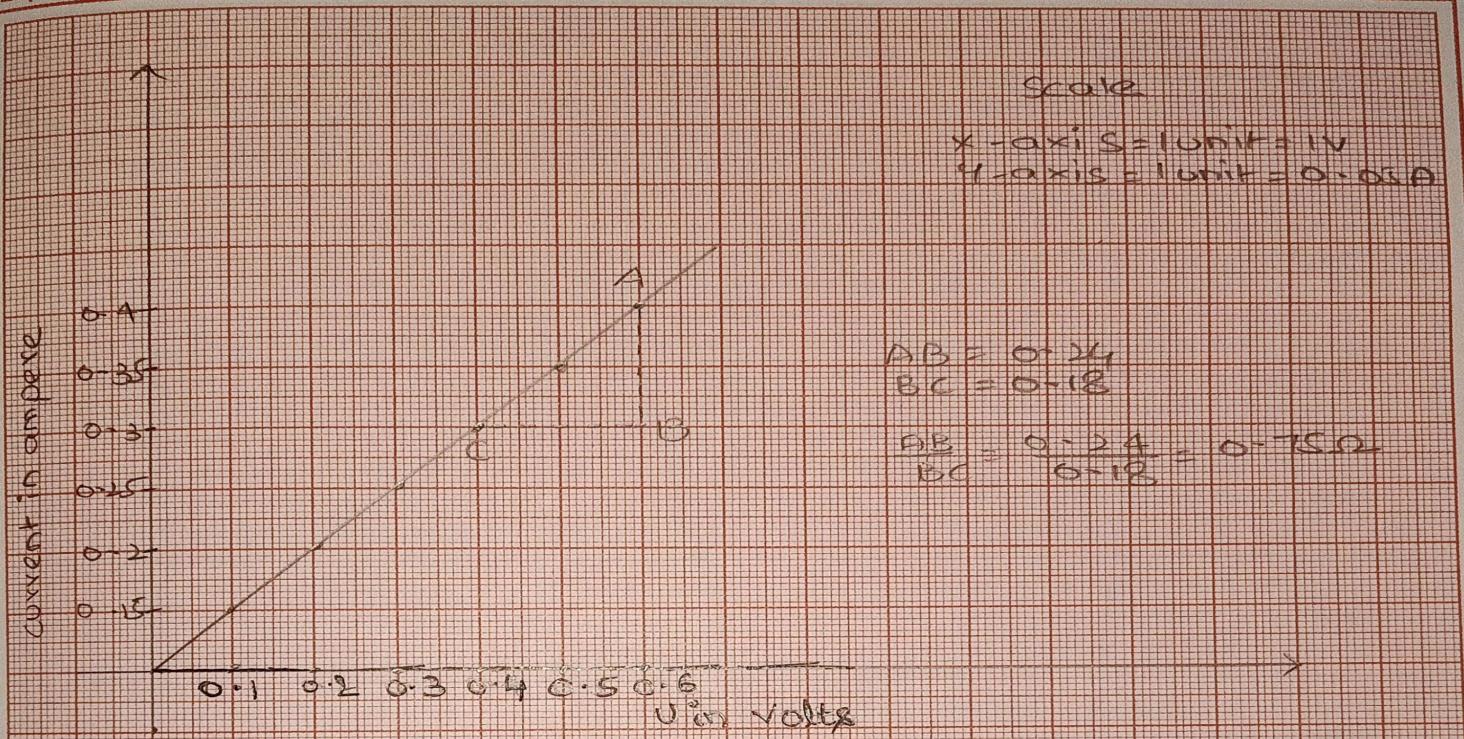

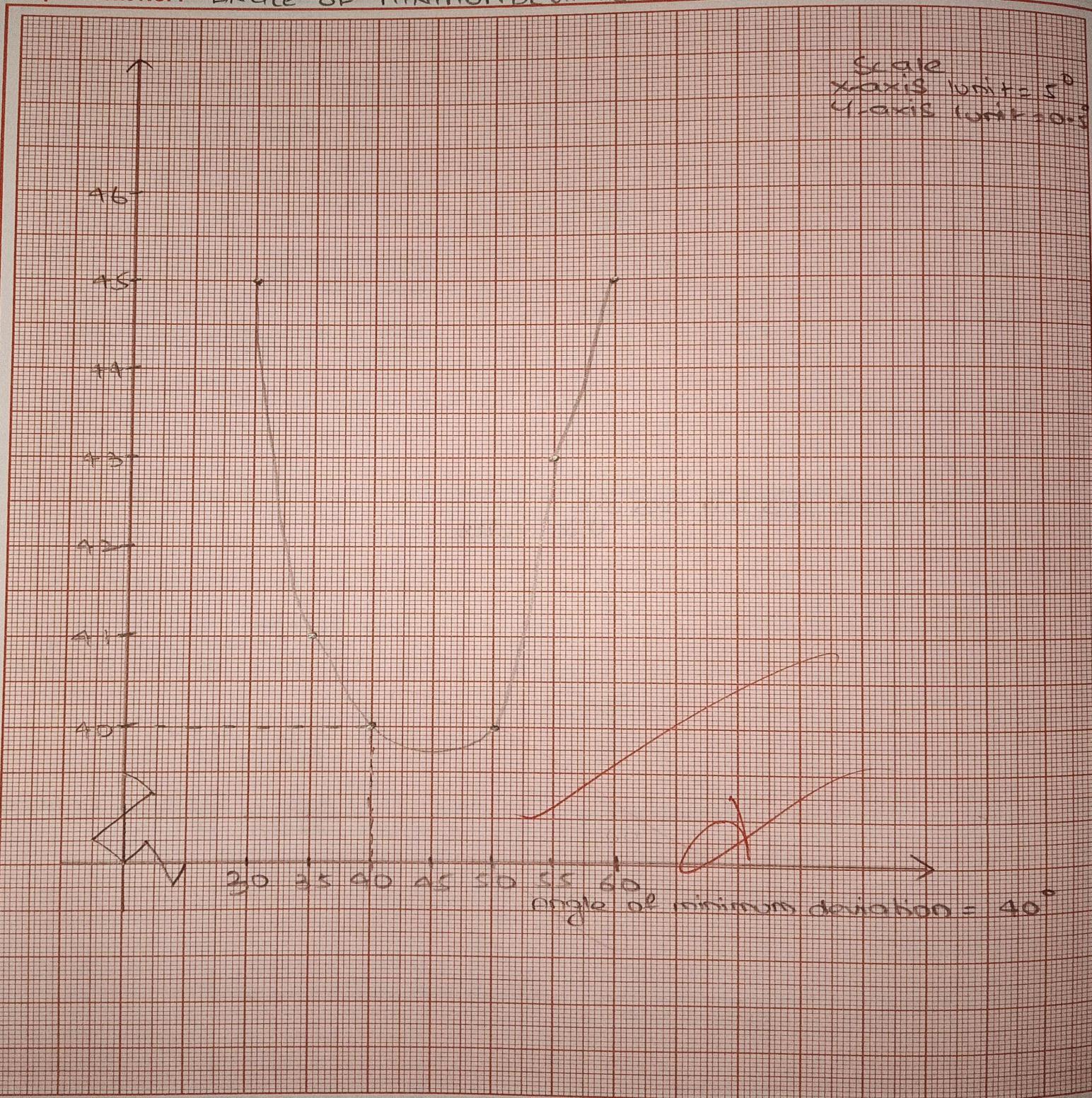Experiment No.: ANGLE OF MINIMUM DEVIATION FOR PRISM Date:




Experiment No. : P-N JUNCTION

Date :

FORWARD BIAS

Scale
xaxis unit = 0.1V
yaxis unit = 1mA

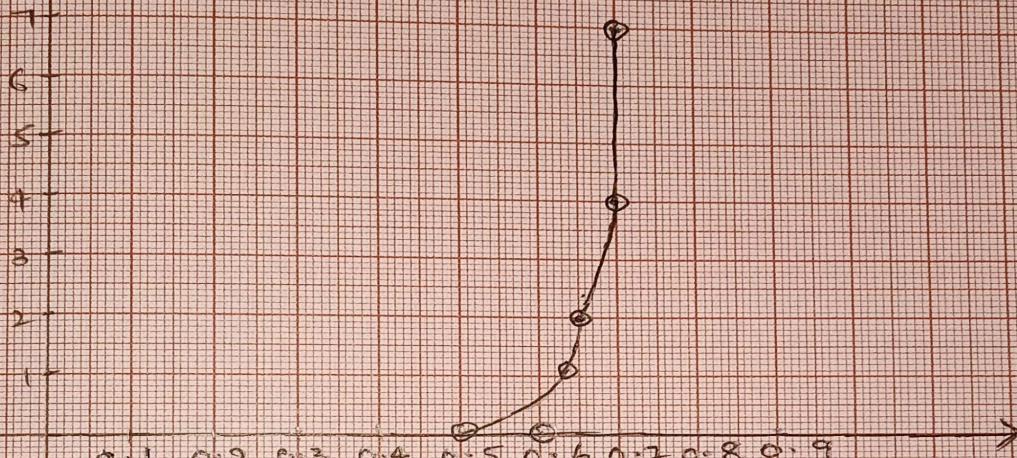

Reverse bias

Cut-in value = 0.6V

Cut-off voltage = 15V

